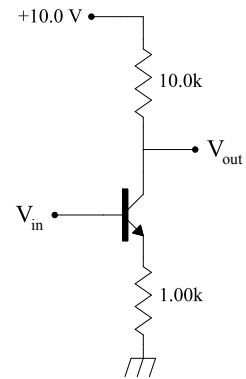


Due Wednesday, September 26

1. The circuit shows a  $10\times$  common emitter amplifier, similar to the one used in Lab 4. Assuming that the transistor has a  $V_{BE}$  diode drop of exactly 0.6 V, a  $V_{CES}$  saturation voltage of 0.2 V, and a current gain  $\beta = 100$ , calculate the output voltage  $V_{out}$  as a function of the input voltage  $V_{in}$ . What are the largest and smallest output voltages that can be obtained, and what input voltage limits correspond to this range?




2. The circuit shown is known as a current mirror. Assume that both transistors are perfectly identical, and take them to be 2N3904's if it matters.

(a) Approximately how much current will flow through the 10 k $\Omega$  resistor?

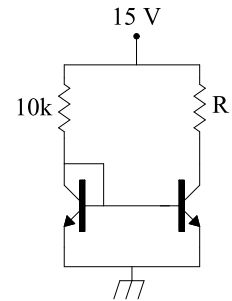(b) Determine the current through the unspecified resistor  $R$  in terms of  $R$  and the other circuit parameters. You can assume that  $R \lesssim 10$  k $\Omega$ .

Can you see why this is called a current mirror?



3. (i) Recall that pnp transistors work like npn transistors with the current directions reversed. Circuit (a) shows a pnp transistor being used as an emitter follower; compare to Fig. 4.4(b) in your lab manual. If  $V_{in}$  is a 10 V<sub>pp</sub> sine wave with no dc offset, sketch  $V_{out}(t)$  on a reasonably accurate vertical scale.

(ii) An npn transistor and a pnp transistor can be combined as shown in (b). Sketch the output of this circuit for the same input as part (i). (This circuit is called a push-pull follower, and shows one way to deal with the base-biasing problem.)

