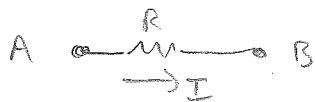


Lecture 1: Ohm's Law

Describes resistors



$$V_A - V_B = IR$$

V in volts

I in amps

R in ohms


Note direction for positive I matters

Need to show on diagram. $I < 0 \Rightarrow$ current flows opposite arrow

Often write $V = IR$, but be careful

V is really ΔV


Example:

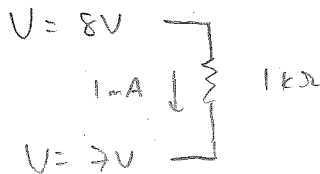

$IR = 1V$, but no point in circuit at $V = 1V$


• Rules for combining resistors:

Series:

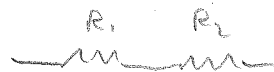

$$R_{TOT} = R_1 + R_2$$

Parallel:

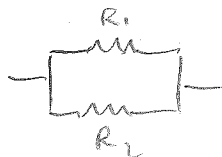


$$\frac{1}{R_{TOT}} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$R_{TOT} = \frac{R_1 R_2}{R_1 + R_2} \equiv R_1 || R_2$$

In fact, any network of resistors between two points is equivalent to a single R_{TOT}

\rightarrow Thevenin's Theorem (one version)

Example:

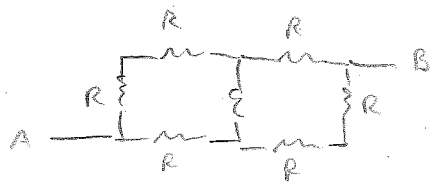


$$\equiv A \text{ --- } R_{TOT} \text{ --- } B$$

$$R_{TOT} = \frac{7}{5} R$$

Solve by setting up $\Delta V = IR$ for each resistor, solve simultaneous equations.

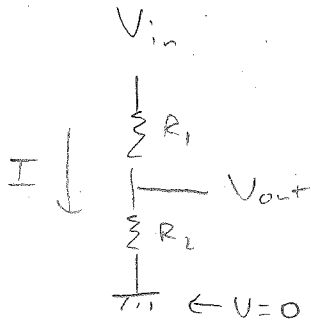• Important building block for electronics: Voltage Divider



Solve for V_{out} :

$$I = \frac{V_{in}}{R_{TOT}} = \frac{V_{in}}{R_1 + R_2}$$


$$V_{out} = IR_2 = V_{in} \frac{R_2}{R_1 + R_2}$$

So $V_{out} \propto V_{in}$, attenuated by factor $\frac{R_2}{R_1 + R_2}$

Useful when you need to reduce a voltage

Will also generalize to other types of circuits

Can also have "three-point" divider:

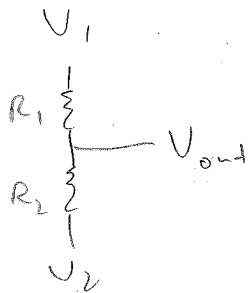

Get

$$V_{out} = \frac{V_1 R_2 + V_2 R_1}{R_1 + R_2}$$

• Power dissipated by resistor $P = IV = I^2 R = \frac{V^2}{R}$

If P too large, resistor burns up!

• Next important circuit element: capacitor


$$\frac{V_A}{V_B} = \frac{1}{C}$$

Satisfies

$$\Delta V = \frac{Q}{C} = \frac{1}{C} \int I dt$$

Q = charge

Example:

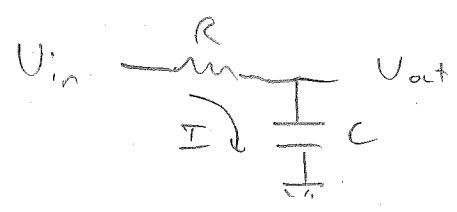


Assume V_{in} initially zero, then apply $V_{in} = \text{const}$

Have $V_{out} = \frac{1}{C} \int I dt \Rightarrow \dot{V}_{out} = \frac{I}{C}$

and $V_{out} = V_{in} - IR$
 $= V_{in} - \dot{V}_{out} RC$

$\Rightarrow RC \dot{V}_{out} + V_{out} = V_{in}$

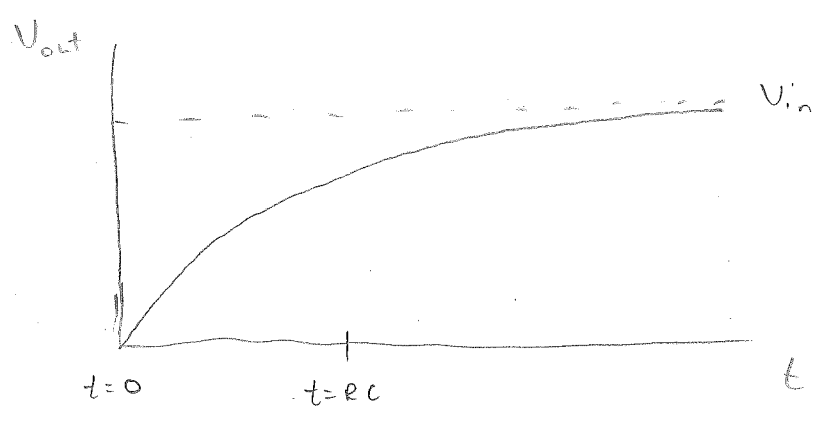Solved by $V_{out}(t) = V_{in} (1 - e^{-t/RC})$



Plumbing analogy:

- Voltage = pressure
- Current = flow
- Resistor = thin tube (friction)
- Capacitor = tank

} useful for intuition