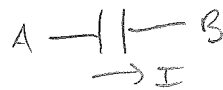


Lecture 2 - Complex Impedance

Last time, introduced capacitors



$$\Delta V = V_A - V_B = \frac{1}{C} \int I dt$$

→ differential eqn relating V & I

Simplifies in particular case of harmonic signals

$$V, I \propto \cos(\omega t + \phi)$$

• Note $\omega \sim \text{rad/s}$ - $\omega = 2\pi f$ $f \sim \text{Hz}$

Convenient to use complex representation

$$V(t) = \text{Re } V e^{i\omega t}$$

$$e^{i\theta} = \cos\theta + i\sin\theta$$

$$\hookrightarrow \text{complex} = |V| e^{i\phi}$$

Assume you know complex numbers

$$\text{So } V(t) = |V| \text{Re } e^{i(\omega t + \phi)} = |V| \cos(\omega t + \phi)$$

$|V|$ = amplitude

ϕ = phase

$$\text{Similarly, } I(t) = \text{Re } I e^{i\omega t}$$

Do calculations with complex form, take real part at end

• What if actual signal isn't harmonic?

$$\text{Use Fourier transform } V(t) = \frac{1}{2\pi} \int V(\omega) e^{i\omega t} d\omega$$

Any reasonable function = sum of harmonic fns

For linear circuits, treat each component separately, add up in end.

Apply to resistors & capacitors

$$\text{Resistors simple: } V(t) = I(t)R$$

$$V e^{i\omega t} = I e^{i\omega t} R$$

$$\boxed{V = IR} \rightarrow \text{now a complex relation!}$$

Capacitors

$$V(t) = \frac{1}{C} \int I(t) dt$$

$$V e^{i\omega t} = \frac{1}{C} \int I e^{i\omega t} dt$$

$$= \frac{1}{C} I \frac{e^{i\omega t}}{i\omega}$$

$$\boxed{V = \frac{1}{i\omega C} I} \Rightarrow |V| = \frac{|I|}{\omega C} \quad \arg V = \arg I - 90^\circ$$

Same form as Ohm's Law: $V = () I$

Here () = complex, freq-dependent but with doesn't care

Generalize Ohm's Law: $V = I Z$


Z = impedance

$\text{Re } Z$ = resistance


$\text{Im } Z$ = reactance

Resistor has $Z = R$ Capacitor has $Z = \frac{1}{i\omega C}$

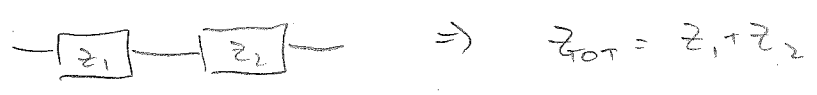With this method, can solve any circuit like resistor network




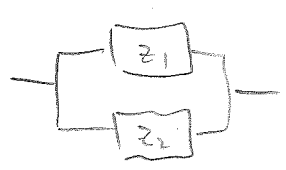
$$\Rightarrow Z_{\text{tot}} = Z_1 + Z_2$$



$$\Rightarrow Z_{\text{tot}} = Z_1 \parallel Z_2 = \frac{Z_1 Z_2}{Z_1 + Z_2}$$

Example:

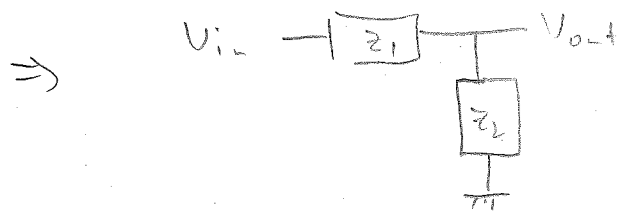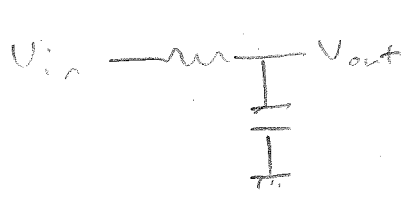

Like voltage divider, solved last time

Use result: $V_{out} = \frac{z_2}{z_1 + z_2} V_{in}$

Here $V_{out} = \frac{\frac{1}{i\omega C}}{R + \frac{1}{i\omega C}} V_{in}$
 $= \frac{1}{1 + i\omega RC} V_{in}$

Amplitude $|V_{out}| = \left| \frac{V_{in}}{1 + i\omega RC} \right| = \frac{|V_{in}|}{\sqrt{1 + \omega^2 R^2 C^2}}$

~ constant for $\omega \ll \frac{1}{RC}$
 decreases for $\omega \gg \frac{1}{RC}$

Functions as low pass filter: attenuates high freq components

Also get phase shift

$\frac{1}{1 + i\omega RC} = \frac{1}{\sqrt{1 + \omega^2 R^2 C^2}} e^{i\phi}$ (polar form $z = |z|e^{i\theta}$)

To get ϕ :

$1 + i\omega RC = \sqrt{1 + \omega^2 R^2 C^2} e^{-i\phi}$
 $= \sqrt{1 + \omega^2 R^2 C^2} (\cos\phi - i\sin\phi)$

So $\cos\phi - i\sin\phi = \frac{1}{\sqrt{1 + \omega^2 R^2 C^2}} + i \frac{\omega RC}{\sqrt{1 + \omega^2 R^2 C^2}}$

$\tan\phi = \frac{\sin\phi}{\cos\phi} = - \frac{\omega RC}{1/\sqrt{}} = -\omega RC$

$\phi = -\tan^{-1}(\omega RC)$


For $\omega \ll \frac{1}{RC}$, $\phi \approx 0$

$\omega \gg \frac{1}{RC}$, $\phi \approx -90^\circ$

All together: $V_{out}(t) = \frac{1}{\sqrt{1 + \omega^2 RC}} e^{i(\omega t + \phi_{in} - \tan^{-1} \omega RC)}$

Discuss a few more components:

2.4

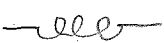• Inductor 

Has $V = L \frac{dI}{dt}$

Impedance $Z = i\omega L$

So for example:



$$\begin{aligned} Z_{TOT} &= Z_1 || Z_2 \\ &= \frac{(i\omega L)(\frac{1}{i\omega C})}{i\omega L + \frac{1}{i\omega C}} \\ &= \frac{i\omega L}{1 - \omega^2 LC} \end{aligned}$$

• Battery




Generates voltage $V_A - V_B = V_{battery}$

Like Ohm's law, only voltage difference is defined

Absolute voltage of either terminal determined by rest of circuit, "floating"

• Transformer

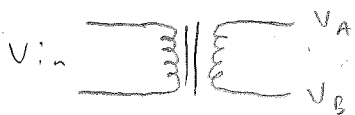

For ac (oscillating) signals:

$$V_A - V_B = k V_{in} \cos \omega t$$

k can be larger, smaller, or equal to 1

Useful to change amplitude

Also, output floats, like a battery