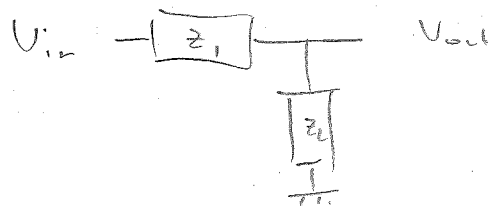


# Lecture 3 - Impedance & Transfer Functions


Recall voltage divider:

$$V_{out} = V_{in} \frac{z_2}{z_1 + z_2}$$



This assumes no current flows from the output:  $I_{out} = 0$

What if  $I_{out} \neq 0$ ?

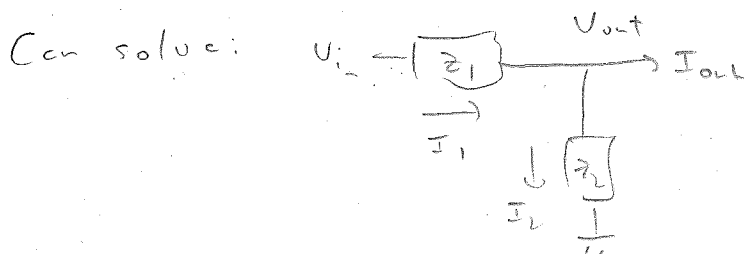

Have

$$I_1 = I_{out} + I_2$$

$$V_{in} - V_{out} = I_1 z_1 \rightarrow V_{in} - V_{out} = \left( I_{out} + \frac{V_{out}}{z_2} \right) z_1$$

$$V_{out} = I_2 z_2$$

$$V_{in} - I_{out} z_1 = V_{out} \left( 1 + \frac{z_1}{z_2} \right)$$

$$V_{out} = \frac{z_2}{z_1 + z_2} V_{in} - I_{out} \frac{z_1 z_2}{z_1 + z_2}$$

So as  $I_{out}$  increases,  $V_{out}$  decreases.

This is a generic effect. Can describe with another version of Thevenin's Theorem:

Any network of sources and impedances acts like a single source  $V_{eff}$  in series with single impedance  $z_{out}$

Here:



Equivalent circuit is easy to analyze:


$$V_{out} = V_{eff} - I_{out} Z_{out}$$

Compare to above, see

$$V_{eff} = V_{in} \frac{z_2}{z_1 + z_2}$$

$$Z_{out} = \frac{z_1 z_2}{z_1 + z_2} = z_1 || z_2$$

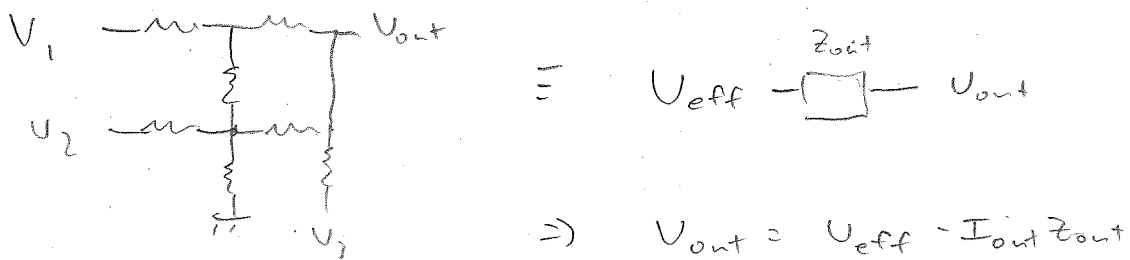This is useful because it applies to any circuit



So for any circuit, output voltage decreases with current

$$Z_{out} = - \frac{dV_{out}}{dI_{out}} = \text{"output impedance"}$$

If you know  $Z_{out}$ , can say how much current can be supplied by a circuit.

Good power supply has low  $Z_{out}$

How to determine  $Z_{out}$ :

- 1) Assume some  $I_{out}$ , and solve for  $V_{out}$ , like we did with divider.
- 2) Easier: Assume  $I_{out} = 0$  and solve for  $V_{out} = V_{eff}$   
Then assume  $V_{out} = 0$  and solve for  $I_{out}(\text{short})$   
Then  $Z_{out} = V_{eff} / I_{out}(\text{short})$

Example:

The example circuit shows a voltage source  $V_{in}$  in series with impedance  $z_1$ . This is followed by a parallel combination of impedance  $z_2$  and a short circuit. The current through the short circuit is  $I_{short}$ .

$$I_{short} = \frac{V_{in}}{z_1}$$


$$\Rightarrow Z_{out} = \frac{(V_{in} \cdot \frac{z_2}{z_1 + z_2})}{V_{in}/z_1} = \frac{z_1 z_2}{z_1 + z_2}$$

3) Good way to measure:

Measure  $V_{\text{eff}} = V_{\text{out}}$  using voltmeter

Hook output to ground through impedance  $Z_L$ ,  
measure  $V_{\text{out}}$  again

Effective circuit:

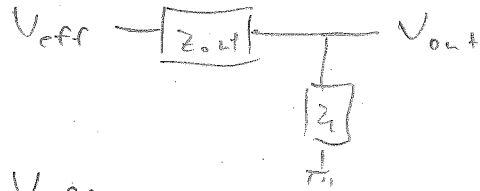

See 
$$V_{\text{out}} = \frac{Z_L}{Z_{\text{out}} + Z_L} V_{\text{eff}}$$

Solve for 
$$Z_{\text{out}} = Z_L \times \frac{V_{\text{out}}}{V_{\text{eff}} - V_{\text{out}}}$$

Some notes:

- Really only applies to linear circuits. Many circuits are non-linear. But can still approximate as linear for (relatively) small  $I_{\text{out}}$
- If  $I_{\text{out}}$  is large, circuit dissipates internal power  $I^2 R_{\text{out}}$ . If too large, circuit can break! Try not to short outputs to ground unless you know circuit can survive.

# Related topic: Input Impedance


Output of any circuit acts like  $V_{eff} - [Z_{out}] - V_{out}$

Input of any circuit acts like  $V_{in} - [Z_{in}] - V_{float}$

$V_{float}$  = voltage present at input if you don't hook anything up. (Generally  $\neq V_{eff}$  (out))

Very often,  $V_{float} = \text{ground}$

Example:

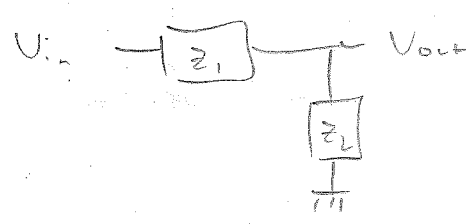


With no  $V_{in}$  source, have  $V_{in} = V_{out} = 0 \Rightarrow V_{float} = 0$


With  $V_{in}$ , have  $I_{in} = \frac{V_{in}}{Z_1 + Z_2} \Rightarrow Z_{in} = Z_1 + Z_2$

Note we assume  $I_{out} = 0$ , because no load is present. If we had a load  $Z_L$ ,  $Z_{in}$  would change.
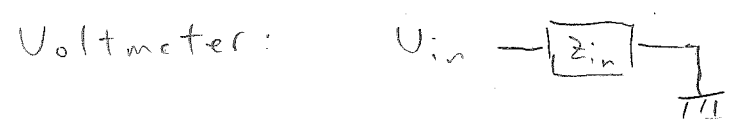
## Input impedance important for measuring instruments



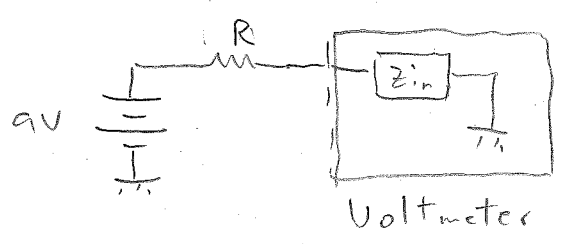Describes fact that some current flows in to device. Can affect measurement:




Forms divider, actually measures

$$V_{meas} = 9V \times \frac{Z_{in}}{Z_{in} + R}$$


Ideally,  $Z_{in} \gg R$ , so  $V_{meas} \rightarrow 9V$

Or in ammeter:

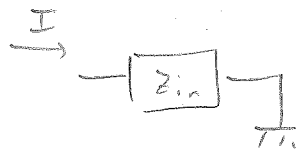

Needs some input voltage  $V_{in} = I Z_{in}$  to operate

For instance:

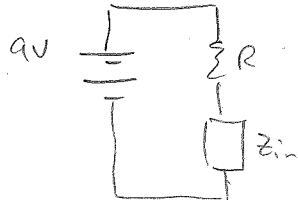

$$I = \frac{9V}{R + Z_{in}}$$

Unless  $Z_{in} \ll R$ ,  $I$  changes when you add ammeter to circuit.

Introduce one more topic, discuss more next time:  
transfer function

Often have relation  $V_{out} = ( ) V_{in}$

divider:  $V_{out} = \frac{Z_2}{Z_1 + Z_2} V_{in}$

In general, write  $V_{out} = G V_{in}$

$G = G(\omega)$  depends on frequency  
Generally complex

Call  $G =$  transfer function

Describes what a circuit does

Often useful to express  $G$  in polar form  $G = |G| e^{i\phi}$

Show using two plots:  $|G|$  vs  $\omega$   
 $\phi$  vs  $\omega$

But  $|G|$  and  $\omega$  typically vary a lot: use log plots  
 $\log |G|$  vs  $\log \omega$  (or  $\log f$ )  
 $\phi$  vs  $\log \omega$

Call pair = Bode plot

Convenient way to describe how circuit functions

$\log|G|$  so convenient, it has a special unit: dB

write

$$g(\text{in dB}) = 20 \log|G|$$

$$\text{So } 20 \text{ dB} \Rightarrow |G| = 10$$

$$-20 \text{ dB} \Rightarrow |G| = 0.1$$

Usually see Bode plot as  $g$  vs  $\log_{10} f$   
 $\phi(\text{deg})$  vs  $\log_{10} f$