

# Lecture 6 - Transistors

Resistors, capacitors, diodes are passive devices


- Apply a voltage, get a current
- Always some power dissipation

Most applications require active components

- Generate or amplify a signal
- Really, transfer power from a supply to a signal

Basic active building block: transistor

Three terminals:

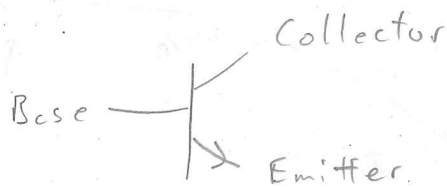

Simple explanation of what it does:


Current amplifier:  $I_{CE} = \beta I_{BE}$

current  
from collector  
to emitter

$\beta \sim 100$  typically

Picture: transistor man adjusts potentiometer

to keep  $I_{CE} = \beta I_{BE}$

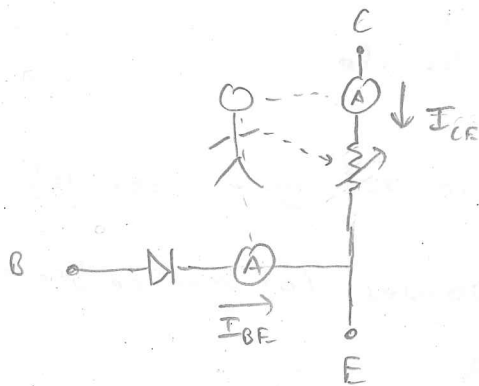


- All he can control is pot setting
- If  $V_C \leq V_E$ , pot is at minimum resistance, current at maximum.

Soy transistor is saturated


- Start saturating if  $V_C - V_E < \sim 1V$
- Completely saturated if  $V_C - V_E < \sim 0.2V$

So in typical circuit:

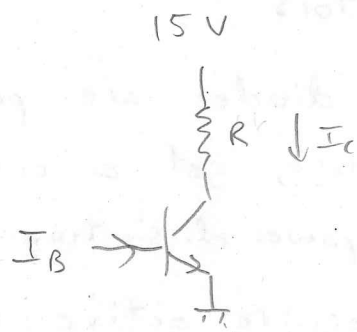

Have  $V_C = 15V - I_C R$

Starts to saturate at  $I_C R = 14V$

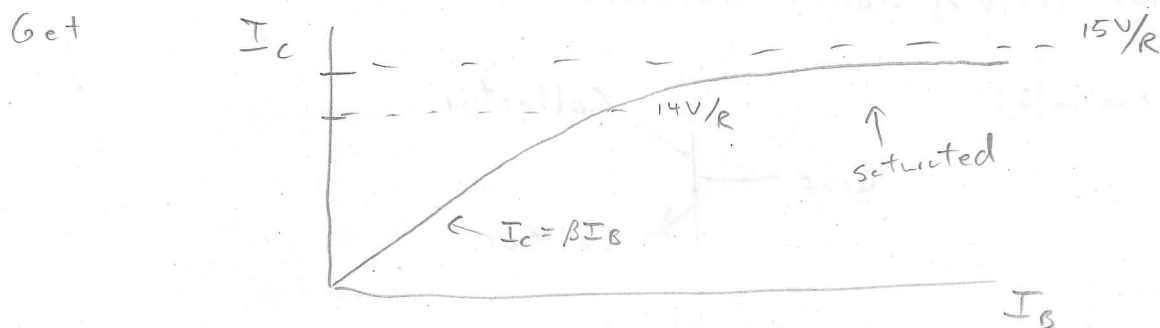

So you can't just count on  $I_C = \beta I_B$

Some more details:

- 1) Looks like diode from B to E (arrow in symbol)

Get diode drop  $V_B \approx V_E + 0.6V$

- 2) Value of  $\beta$  varies from device to device  
+ with temperature

Better to use external components to set gain: see lab

- 3) Limits on  $I_C, I_B, V_{CE}$  & total power (or device breaks)

ZN3904

$$I_C < 200mA$$

$$I_B < 100mA$$

$$V_{CE} < 40V$$


$$P < 500mW$$

Important to consider when designing circuit!

Physics:

Recall diode = pn junction

Transistor = two junctions

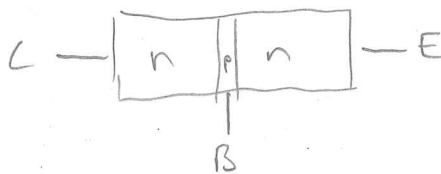


So B-C & B-E really are diodes

Wouldn't expect any current  $C \rightarrow E$

IF  $V_C > V_E$ , get current  $B \rightarrow E$  only

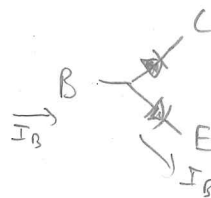$\Rightarrow$  electrons from  $E \rightarrow B$



But, base region is very thin


Electrons that enter through E see positive = attractive potential in C region.  $\sim 99\%$  get diverted into C rather than exiting via B

$\Rightarrow$  current from C to E,  $I_{CE} \approx 100 I_{BE}$

Actually two types of transistor

n-p-n as described

p-n-p:

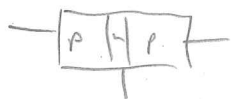

Draw



Very similar, but currents reversed:  $I_{E \rightarrow C} = \beta I_{E \rightarrow B}$

Need  $V_E > V_C$

To remember:

n-p-n: needs positive base

p-n-p: needs negative base

for current gain in normal operation

