

Lecture 10 Op Amp Limitations

Last week focussed on ideal op amp behavior


This week, look at some limitations

One important constraint: output current & voltage are limited

Voltage: V_{out} can't exceed output range

Typically close to supply voltage range


Amplifier looks like

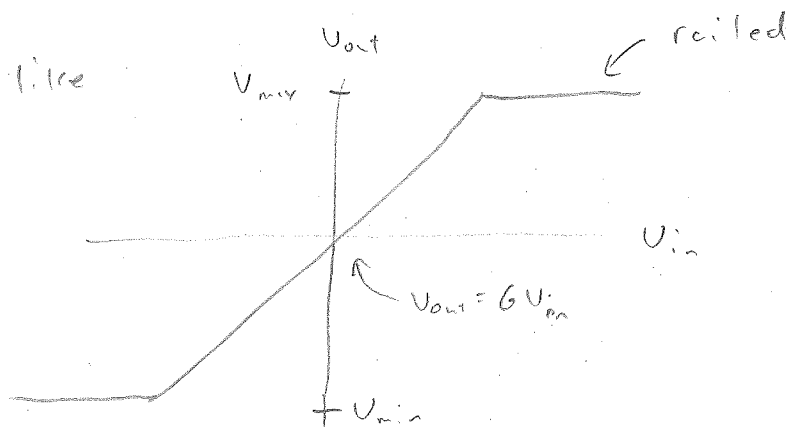

When nominal $V_{out} = 6V_{in}$ exceeds limits,

say that op amp is railed, clamped, clipped, saturated
all same

Current is also limited

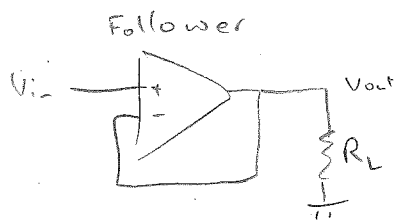

$$V_{out} = V_{in}$$

$$I_{out} = V_{out} / R_L$$


Typically $|I_{max}| \approx 30 \text{ mA}$

If nominal I_{out} is larger, voltage will be clamped at $I_{max} R_L$

So if $R_{load} < \frac{15V}{30mA} = 500\Omega$, op amp is limited by voltage, not current

In many cases, 30 mA is insufficient
Driving motors, speakers, magnet coils
Use transistors to boost current higher


Example:

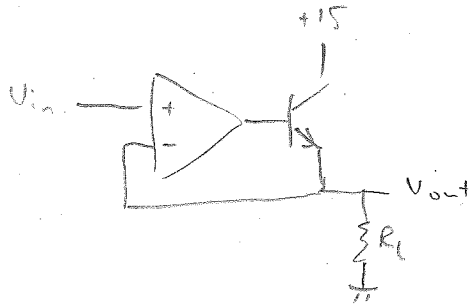


Op amp keeps $V_{out} = V_{in}$, transistor supplies lots of current

In lab, you will plot V_{out} vs I_{out}

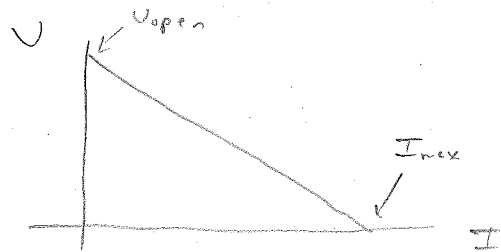Thevenin model predicts $V_{out} = V_{open} - I_{out} Z_{out}$




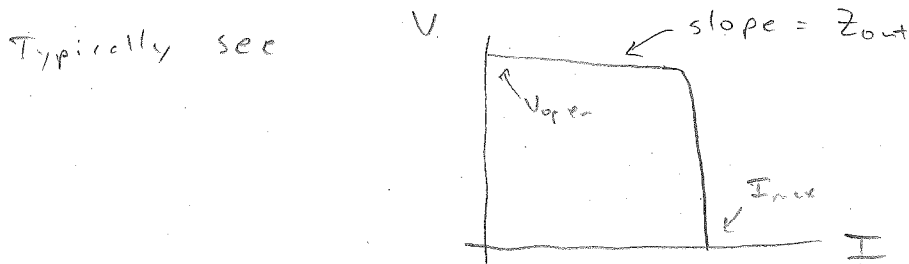But op amps (d most real supplies) aren't linear



Get very small Z_{out} ,
but max current
still limited

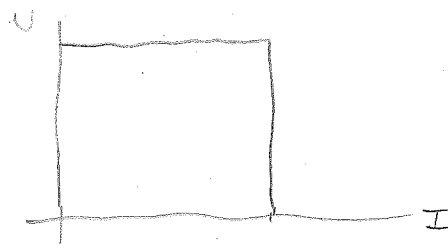Often easiest to approximate as "box": $Z_{out} \approx 0$



V_{out} indep of I for $I \leq I_{max}$
~ ideal source