

Lecture 15 Flip Flops


Two classes of logic circuit

Combinatoric: output determined by input

Sequential: output depends on history

Considered combinatoric circuits last week

Simple sequential circuit:

 

Analyze:

Suppose $S=L$

Then $Q=H$, regardless of A

If $S=H$, then Q depends on A

$Q=L$ if $A=H$

$Q=H$ if $A=L$

S	R	Q
L	L	H
L	H	H
H	L	L
H	H	Q

Now if $R=L$, then $A=H \Rightarrow Q=L$

If $R=H$, two possibilities:

if $Q=H$ then $A=L \Rightarrow Q=H$

if $Q=L$ then $A=H \Rightarrow Q=L$

Both consistent, circuit is bistable

So if $S=R=H$, Q holds whatever value it has

This type of circuit often called a latch:

use S & R to put Q in a given state, then it stays there
 = simple form of memory


Example:

- Set R low
- Apply data D to S : $Q \rightarrow \bar{D}$ (whatever D is)
- Set R & S high, Q holds value \bar{D} indefinitely


More convenient version:

D-type flip flop

19.2

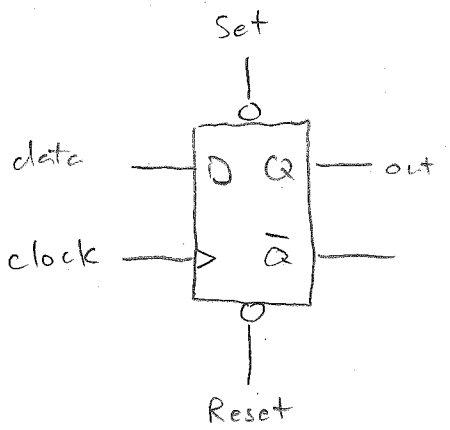

Idea:

When clock signal rises: 
 value at D is stored in Q
 Otherwise D and clock are ignored.
 R & S force Q to L or H,
 indep of D & clock

Truth table:


\bar{S}	\bar{R}	CLK	D	Q
L	X	X	X	H
H	L	X	X	L
H	H	↑	D	D
H	H	X	X	Q

"X" = doesn't matter


Using clock signal as trigger makes it easy to define when data is saved.

Useful for many things

Simplest:

 

Every time CLK ↑, output changes state

 


Divides clock frequency in half

Alternately, forms two-bit counter:

Cycle	\bar{Q}	CLK	Binary
	0	0	0
	1	1	3
	1	0	2
	0	1	1
	0	0	0

Counts down from 3 and then repeats
(to count up, invert both bits)

 Can cascade circuits to make bigger counter:




C	B	A	Binary
1	1	1	7
1	1	0	6
1	0	1	5
1	0	0	4
0	1	1	3
0	1	0	2
0	0	1	1
0	0	0	0
1	1	1	7

Counters are important: have lab on them next week

More generally, counters are example of state machine
= triggered circuit that moves from one state
to another in a defined way

Generally:

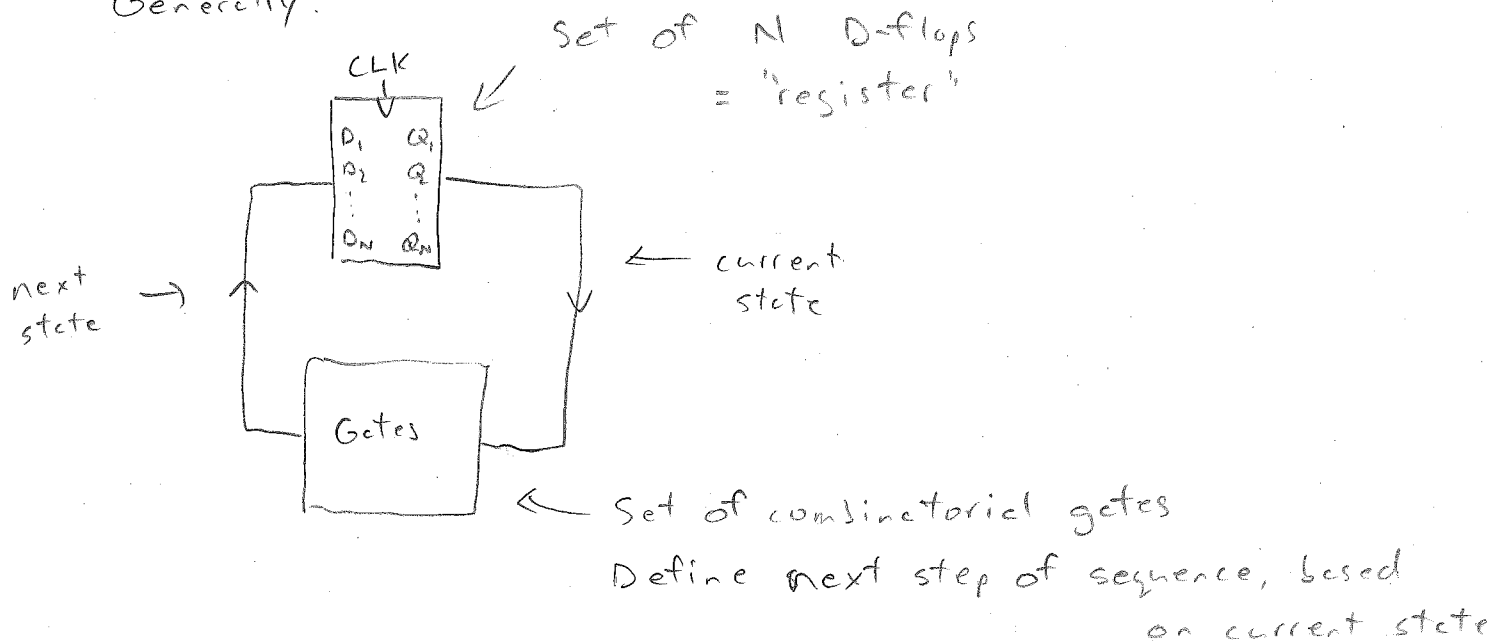

Can use state machine as general purpose computer

For instance, if you want to add two numbers

- 1) Load numbers as initial data
- 2) Cycle through sequence of steps leading to
- 3) Output = sum of inputs

Can implement any sequence of logical steps
= program

Discuss further next time.