

Real world signals are generally analog

Need to convert analog  $\rightarrow$  digital for measurements "ADC"

convert digital  $\rightarrow$  analog for control "DAC"

Many methods.

Simplest: comparator



Like op-amp without feedback

If  $V_+ > V_-$ ,  $V_{out} = + \text{supply}$

$V_+ < V_-$ ,  $V_{out} = - \text{supply}$

Make supply voltages  $+5V, 0V$ :

get one-bit ADC

Or make  $V_- = 2.5V$ , supplies = desired analog levels

set one-bit DAC


Often, one bit is sufficient

Just need yes/no answer  
or do/don't command


When more than one bit is required, use fancier techniques

DAC = digital to analog converter


Common method = R-2R ladder

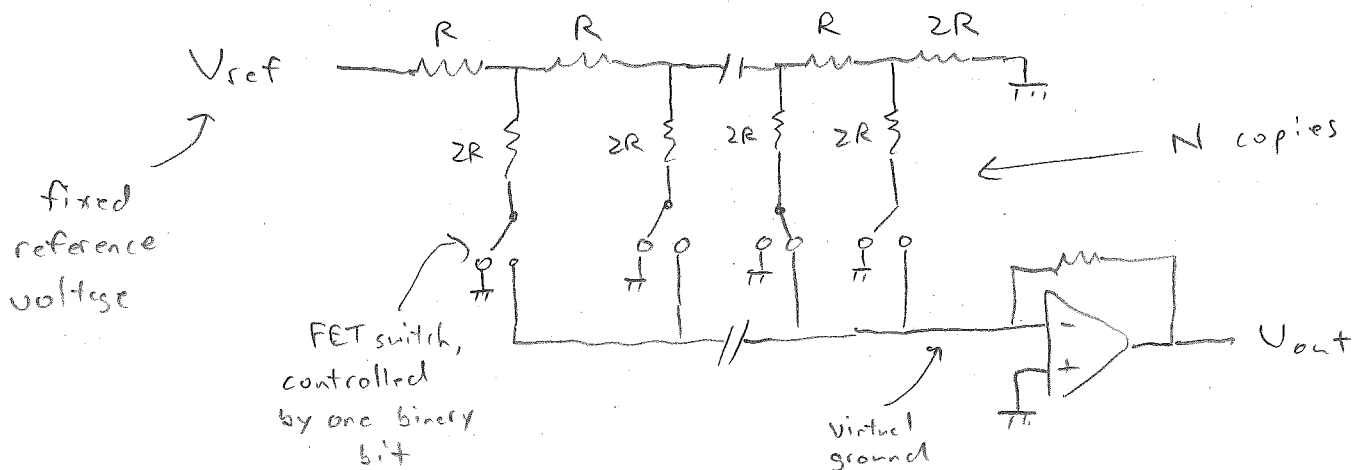


Input network acts like:

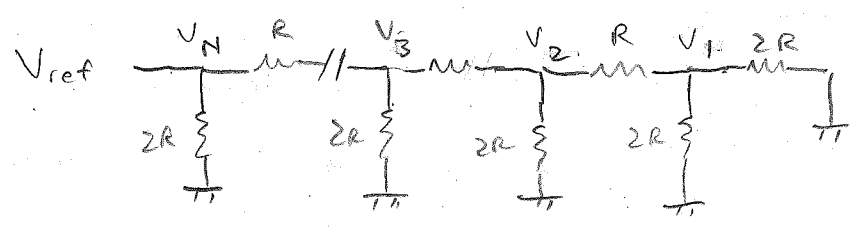

Compute  $V_2 = V_1$

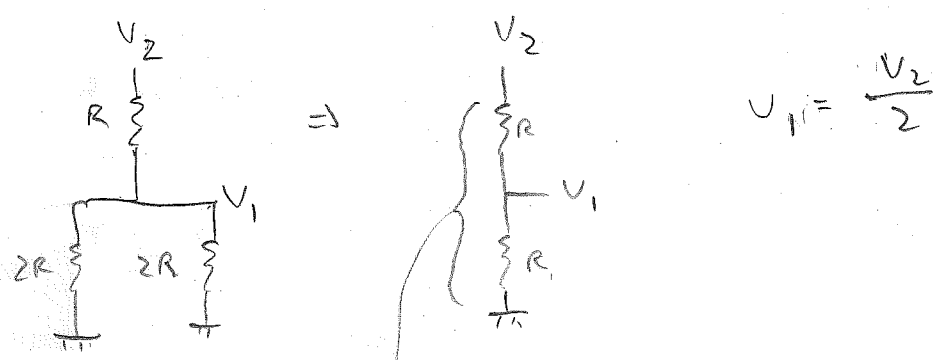

Compute  $V_3 = V_2$

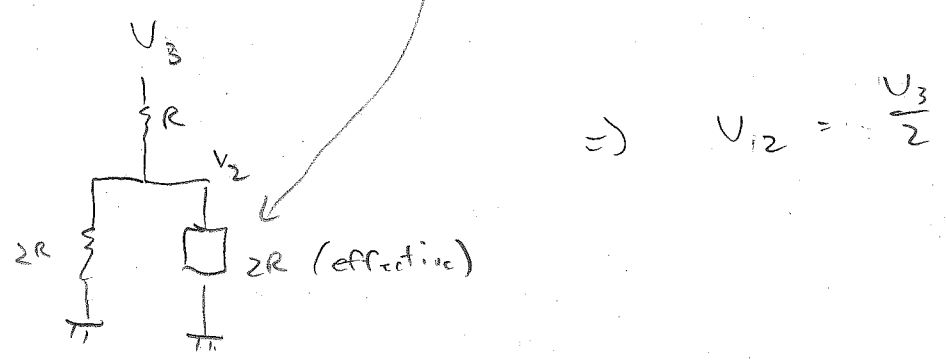

Same for each stage:


$$V_{n+1} = 2V_n \quad n = 1 \text{ to } N-1$$

$$= 2^n V_1$$

So  $V_N = 2^{N-1} V_1$ , but  $V_N = V_{ref}$

$$\Rightarrow V_1 = \frac{V_{ref}}{2^{N-1}}, \quad V_n = \frac{V_{ref}}{2^{N-n}}$$

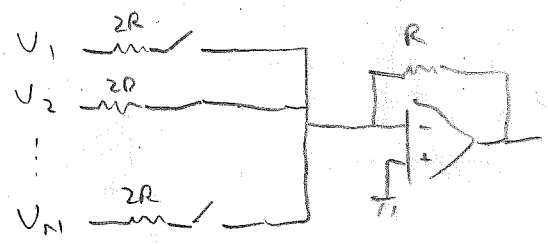Now, op amp is configured as summing amplifier with gain  $1/2$



Say  $b_n$  = bit value for  $n$ th stage

$$b_n = 0 \text{ or } 1$$

$$\begin{aligned} \text{Then } V_{\text{out}} &= \frac{1}{2} \times \sum_{n=1}^N b_n \cdot V_n = \frac{1}{2} \sum_{n=1}^N b_n \frac{V_{\text{ref}}}{2^{N-n}} \\ &= \frac{V_{\text{ref}}}{2^N} \sum_{n=1}^N b_n 2^{n-1} \end{aligned}$$

Now  $\sum_n b_n 2^n$  is just binary value of  $\{b_n\}$

$$b_1 = 1\text{s place}$$

$$b_2 = 2\text{s place}$$

$$b_3 = 4\text{s place} \quad \text{etc}$$

$$\text{So } V_{\text{out}} = \Delta V \times \text{value} \{b_n\}$$

$$\Delta V = \frac{V_{\text{ref}}}{2^N} = \text{minimum voltage step}$$

So if  $N=10$  (values = 0 to 1023)

and  $\Delta V = 1\text{mV}$ , can get output value from  
0 to 1.023 V  
as specified by data

Typical values are  $N=8, 12, 16$

$$V_{\text{ref}} > 1 \text{ to } 10 \text{ V}$$

$\Delta V =$  voltage resolution

typically 1 to 10 mV

ADC = analog to digital converter

measure voltage  $V$ , output binary values  $\{b_n\}$

with value  $\{b_n\} = \frac{V}{\Delta V}$


Larger  $N \Rightarrow$  more bits  $\Rightarrow$  smaller  $\Delta V \Rightarrow$  more resolution

Three common techniques:

- Flash: accurate & very fast, but limited to small  $N$   
Often used for digital scopes
- Integrating: very accurate but slow, works at large  $N$   
Often used for digital voltmeters
- Successive Approximation: fairly fast & fairly accurate  
 $\Rightarrow$  medium  $N$

Common general purpose method

Technique:

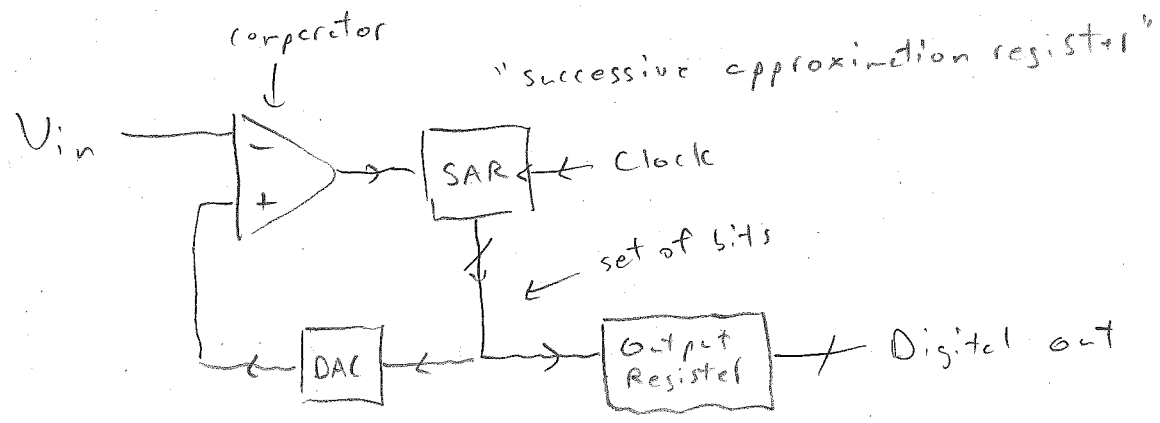

SAR generates one bit at a time

Initial output = middle of range = "guess" for right value

DAC converts to voltage in middle of range

Comparator says whether guess is high or low

If guess is high, SAR rises to middle of upper half

low, SAR drops to middle of lower half

repeat  
 $N$   
times

Clock controls timing for new guesses

Register holds output until conversion complete

Each cycle gives one more bit

Example:  $N = 8$      $V_{ref} = 5 \text{ V}$      $\Rightarrow$      $\Delta V = \frac{5}{2^8} = 19.5 \text{ mV}$


So  $V_{in} = 1.330 \text{ V}$

Cycle	guess	Value	DAC	Comparator
1	1000 0000	128	2.496 V	H
2	0100 0000	64	1.248 V	L
3	0110 0000	96	1.872 V	H
4	0101 0000	80	1.560 V	H
5	0100 1000	72	1.404 V	H
6	0100 0100	68	1.326 V	L
7	0100 0110	70	1.365 V	H
8	0100 0101	69	1.346 V	H

Final output either 0100 0101  
or 0100 0100, depending on  
circuit details

Might worry: what if  $V_{in}$  changes during measurement?

Solve with "sample and hold" circuit

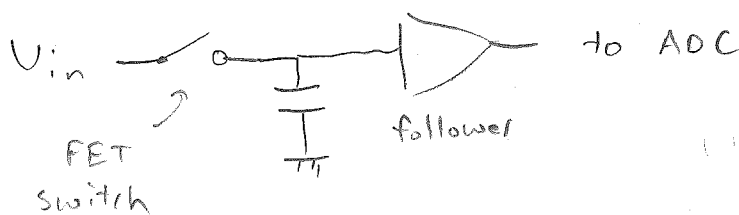

When switch is open, voltage on ADC held  $\approx$  constant

Important for all ADC techniques